
Organización de Computadoras – Fac. de Informática – Prof. Jorge Runco Curso 2020 - Práctica 4 – Lógica y Compuertas

6)

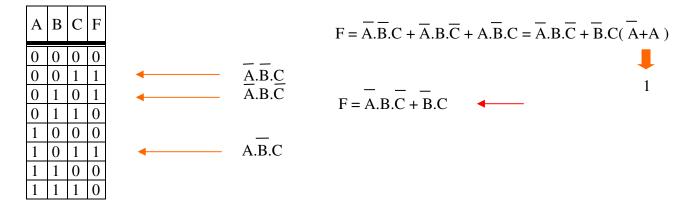

7) Segmento f

A	В	С	D	Decimal	f
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	2	0
0	0	1	1	3	0
0	1	0	0	4	1
0	1	0	1	5	1
0	1	1	0	6	1
0	1	1	1	7	0
1	0	0	0	8	1
1	0	0	1	9	1
1	0	1	0	-	0
1	0	1	1	-	0
1	1	0	0	-	0
1	1	0	1	-	0
1	1	1	0	-	0
1	1	1	1	-	0