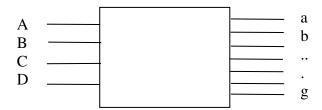


Organización de Computadoras – Fac. de Informática – Prof. Jorge M. Runco Curso 2020 - Práctica 4 – Lógica y compuertas



Decimal	A	В	C	D	a	••••	g	
0	0	0	0	0	1		0	
1	0	0	0	1	0		0	
2	0	0	1	0	1		1	•
3	0	0	1	1	1		1	•
4	0	1	0	0	0		1	•
5	0	1	0	1	1		1	4
6	0	1	1	0	1		1	4
7	0	1	1	1	1		0	
8	1	0	0	0	1		1	•
9	1	0	0	1	1		1	4
	1	0	1	0	0		0	
	1	0	1	1	0		0	
	1	1	0	0	0		0	
	1	1	0	1	0		0	
	1	1	1	0	0		0	
	1	1	1	1	0		0	

$$g = \overline{ABCD} + \overline{ABCD}$$